

# Introduction to Electrical Circuits

**Final Term**

**Week: 9**

**Faculty Name: Dr. Md. Kamrul Hassan**

**Email ID: [mdkamrul@aiub.edu](mailto:mdkamrul@aiub.edu)**

**Room No: D0414**

**Book**



**Introductory Circuit Analysis**

Robert L. Boylestad  
Eleventh Edition

# Series Parallel Network Analysis

For the network in Fig. 16.1:

- Calculate  $\mathbf{Z}_T$ .
- Determine  $\mathbf{I}_s$ .
- Calculate  $\mathbf{V}_R$  and  $\mathbf{V}_C$
- Find  $\mathbf{I}_C$ .
- Compute the power delivered.
- Find  $F_p$  of the network.

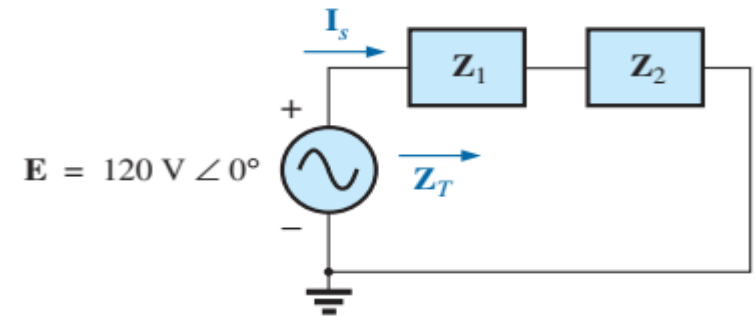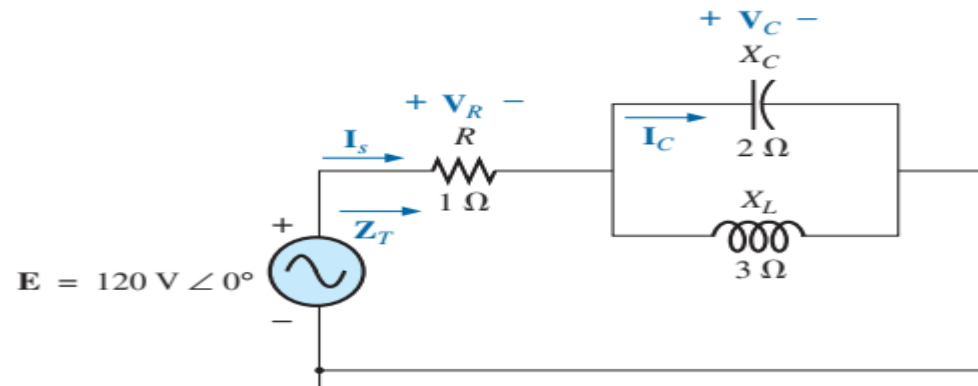

**FIG. 16.2**

Network in Fig. 16.1 after assigning the block impedances

**Solutions:**

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2$$

with

$$\mathbf{Z}_1 = R \angle 0^\circ = 1 \Omega \angle 0^\circ$$

$$\begin{aligned} \mathbf{Z}_2 = \mathbf{Z}_C \parallel \mathbf{Z}_L &= \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(2 \Omega \angle -90^\circ)(3 \Omega \angle 90^\circ)}{-j2 \Omega + j3 \Omega} \\ &= \frac{6 \Omega \angle 0^\circ}{j1} = \frac{6 \Omega \angle 0^\circ}{1 \angle 90^\circ} = 6 \Omega \angle -90^\circ \end{aligned}$$

and

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 1 \Omega - j6 \Omega = 6.08 \Omega \angle -80.54^\circ$$

$$\text{b. } \mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{120 \text{ V} \angle 0^\circ}{6.08 \Omega \angle -80.54^\circ} = 19.74 \text{ A} \angle 80.54^\circ$$

- Referring to Fig. 16.2, we find that  $\mathbf{V}_R$  and  $\mathbf{V}_C$  can be found by a direct application of Ohm's law:

$$\mathbf{V}_R = \mathbf{I}_s \mathbf{Z}_1 = (19.74 \text{ A} \angle 80.54^\circ)(1 \Omega \angle 0^\circ) = 19.74 \text{ V} \angle 80.54^\circ$$

$$\begin{aligned} \mathbf{V}_C &= \mathbf{I}_s \mathbf{Z}_2 = (19.74 \text{ A} \angle 80.54^\circ)(6 \Omega \angle -90^\circ) \\ &= 118.44 \text{ V} \angle -9.46^\circ \end{aligned}$$

- Now that  $\mathbf{V}_C$  is known, the current  $\mathbf{I}_C$  can also be found using Ohm's law.

$$\mathbf{I}_C = \frac{\mathbf{V}_C}{\mathbf{Z}_C} = \frac{118.44 \text{ V} \angle -9.46^\circ}{2 \Omega \angle -90^\circ} = 59.22 \text{ A} \angle 80.54^\circ$$

$$\text{e. } P_{\text{del}} = I_s^2 R = (19.74 \text{ A})^2 (1 \Omega) = 389.67 \text{ W}$$

$$\text{f. } F_p = \cos \theta = \cos 80.54^\circ = 0.164 \text{ leading}$$

# Series Parallel Network Analysis

**EXAMPLE 16.3** For the network in Fig. 16.5:

- Calculate the voltage  $V_C$  using the voltage divider rule.
- Calculate the current  $I_s$ .

## Solutions:

- The network is redrawn as shown in Fig. 16.6, with

$$Z_1 = 5 \Omega = 5 \Omega \angle 0^\circ$$

$$Z_2 = -j 12 \Omega = 12 \Omega \angle -90^\circ$$

$$Z_3 = +j 8 \Omega = 8 \Omega \angle 90^\circ$$

$$V_C = \frac{Z_2 E}{Z_1 + Z_2} = \frac{(12 \Omega \angle -90^\circ)(20 \text{ V} \angle 20^\circ)}{5 \Omega - j 12 \Omega} = \frac{240 \text{ V} \angle -70^\circ}{13 \angle -67.38^\circ} = 18.46 \text{ V} \angle -2.62^\circ$$


$$\text{b. } I_1 = \frac{E}{Z_3} = \frac{20 \text{ V} \angle 20^\circ}{8 \Omega \angle 90^\circ} = 2.5 \text{ A} \angle -70^\circ$$

$$I_2 = \frac{E}{Z_1 + Z_2} = \frac{20 \text{ V} \angle 20^\circ}{13 \Omega \angle -67.38^\circ} = 1.54 \text{ A} \angle 87.38^\circ$$


and

$$\begin{aligned} I_s &= I_1 + I_2 \\ &= 2.5 \text{ A} \angle -70^\circ + 1.54 \text{ A} \angle 87.38^\circ \\ &= (0.86 - j 2.35) + (0.07 + j 1.54) \end{aligned}$$

$$I_s = 0.93 - j 0.81 = 1.23 \text{ A} \angle -41.05^\circ$$

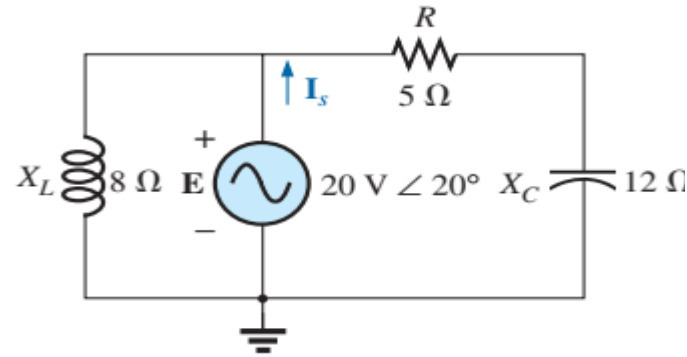

**FIG. 16.5**  
Example 16.3.

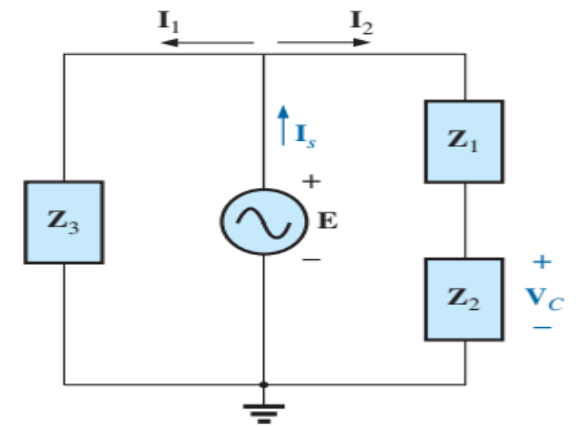

**FIG. 16.6**  
Network in Fig. 16.5 after assigning the block impedances.

# Series Parallel Network Analysis

Example: 16.7

- Compute  $\mathbf{I}$ .
- Find  $\mathbf{I}_1$ ,  $\mathbf{I}_2$ , and  $\mathbf{I}_3$ .
- Verify Kirchhoff's current law by showing that

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$$

- Find the total impedance of the circuit.

**Solutions:**

- Redrawing the circuit as in Fig. 16.15 reveals a strictly parallel network where

$$\mathbf{Z}_1 = R_1 = 10 \Omega \angle 0^\circ$$

$$\mathbf{Z}_2 = R_2 + jX_{L_1} = 3 \Omega + j4 \Omega$$

$$\mathbf{Z}_3 = R_3 + jX_{L_2} - jX_C = 8 \Omega + j3 \Omega - j9 \Omega = 8 \Omega - j6 \Omega$$

The total admittance is

$$\mathbf{Y}_T = \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3$$


$$= \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} = \frac{1}{10 \Omega} + \frac{1}{3 \Omega + j4 \Omega} + \frac{1}{8 \Omega - j6 \Omega}$$

$$= 0.1 \text{ S} + \frac{1}{5 \Omega \angle 53.13^\circ} + \frac{1}{10 \Omega \angle -36.87^\circ}$$

$$= 0.1 \text{ S} + 0.2 \text{ S} \angle -53.13^\circ + 0.1 \text{ S} \angle 36.87^\circ$$


$$= 0.1 \text{ S} + 0.12 \text{ S} - j0.16 \text{ S} + 0.08 \text{ S} + j0.06 \text{ S}$$

$$= 0.3 \text{ S} - j0.1 \text{ S} = 0.316 \text{ S} \angle -18.435^\circ$$

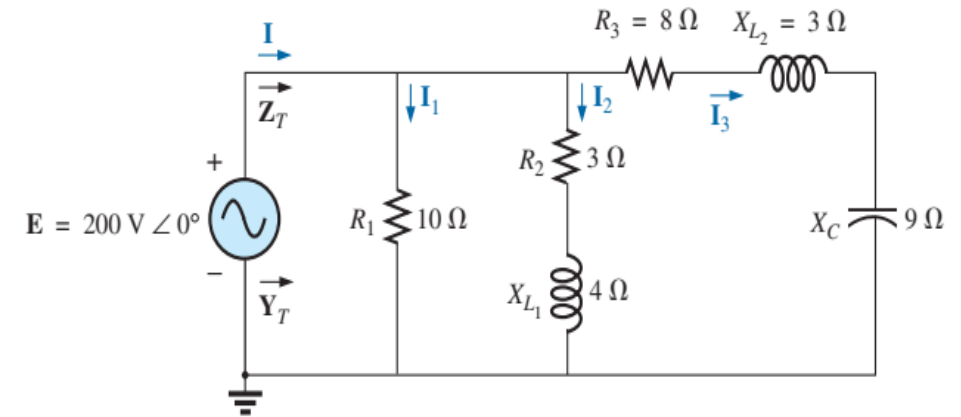

**FIG. 16.14**

Example 16.7.

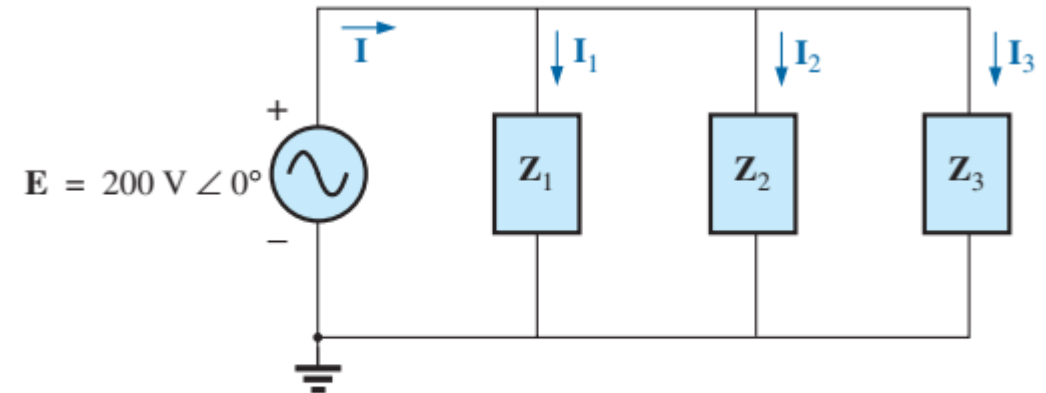

**FIG. 16.15**

Network in Fig. 16.14 following the assignment of the subscripted impedances

# Real Power, Reactive Power and Apparent Power Measurement

## General Equation:

For any system such as in Fig. 19.1, the power delivered to a load at any instant is defined by the product of the applied voltage and the resulting current; that is,

$$p = vi$$

In this case, since  $v$  and  $i$  are sinusoidal quantities, let us establish a general case where

$$v = V_m \sin(\omega t + \theta)$$

and

$$i = I_m \sin \omega t$$

The chosen  $v$  and  $i$  include all possibilities because, if the load is purely resistive,  $\theta = 0^\circ$ . If the load is purely inductive or capacitive,  $\theta = 90^\circ$  or  $\theta = -90^\circ$ , respectively. For a network that is primarily inductive,  $\theta$  is positive ( $v$  leads  $i$ ). For a network that is primarily capacitive,  $\theta$  is negative ( $i$  leads  $v$ ).

$$p = V_m I_m \sin \omega t \sin(\omega t + \theta) \quad (19.1)$$


Applying the trigonometric product-to-sum identity of:  $\sin A \sin B = \frac{\cos(A-B) - \cos(A+B)}{2}$

$$p = VI \cos \theta (1 - \cos 2\omega t) + VI \sin \theta (\sin 2\omega t)$$

where  $V$  and  $I$  are the rms values.

If Eq. (19.1) is expanded to the form

$$p = \underbrace{VI \cos \theta}_{\text{Average}} - \underbrace{VI \cos \theta}_{\text{Peak}} \underbrace{\cos 2\omega t}_{2x} + \underbrace{VI \sin \theta}_{\text{Peak}} \underbrace{\sin 2\omega t}_{2x}$$

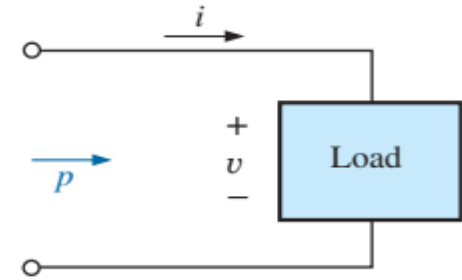

**FIG. 19.1**

*Defining the power delivered to a load.*

# Resistive Circuit

## Resistive Load

For a purely resistive circuit (such as that in Fig. 19.2),  $v$  and  $i$  are in phase, and  $\theta = 0^\circ$ , as appearing in Fig. 19.3. Substituting  $\theta = 0^\circ$  into Eq. (19.1), we obtain

$$\begin{aligned} p_R &= VI \cos(0^\circ)(1 - \cos 2\omega t) + VI \sin(0^\circ) \sin 2\omega t \\ &= VI(1 - \cos 2\omega t) + 0 \end{aligned}$$

$$p_R = VI - VI \cos 2\omega t$$


where  $VI$  is the average or dc term and  $-VI \cos 2\omega t$  is a negative cosine wave with twice the frequency of either input quantity ( $v$  or  $i$ ) and a peak value of  $VI$ .

*the total power delivered to a resistor will be dissipated in the form of heat.*

The **average (real) power** from Eq. (19.2), or Fig. 19.3, is  $VI$ ; or, as a summary,

$$P = VI = \frac{V_m I_m}{2} = I^2 R = \frac{V^2}{R} \quad (\text{watts, W})$$

The energy dissipated by the resistor ( $W_R$ ) over one full cycle  $W = Pt$  where  $P$  is the average value and  $t$  is the period of the applied voltage;

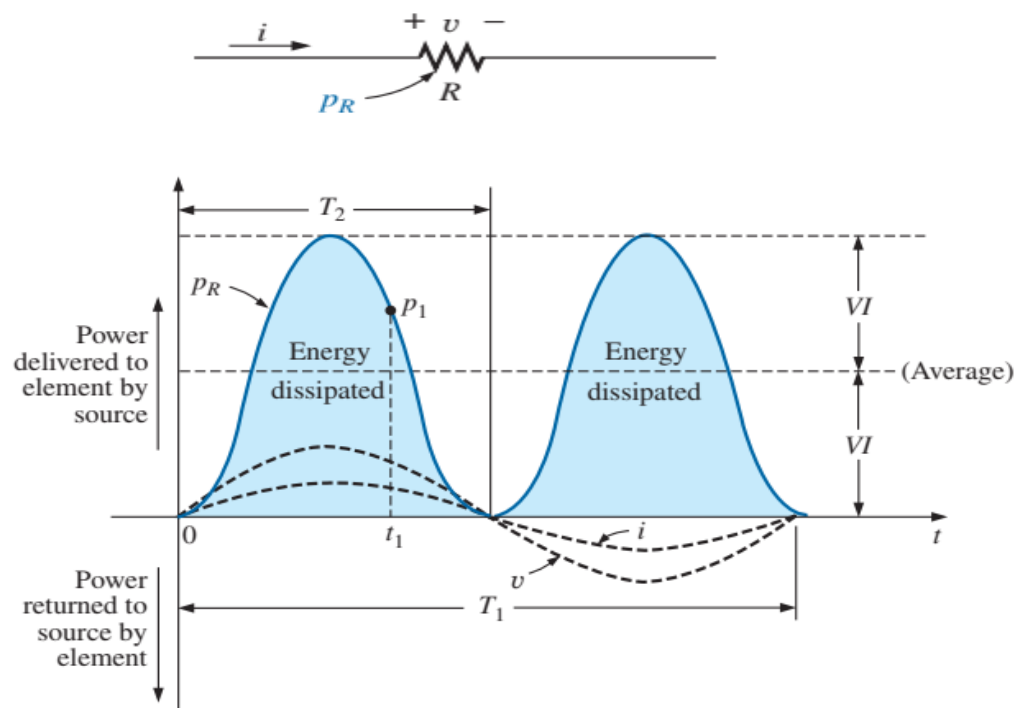

**FIG. 19.3**

*Power versus time for a purely resistive load.*

$$W_R = VIT_1 \quad (\text{joules, J})$$

$$W_R = \frac{VI}{f_1} \quad (\text{joules, J})$$

# Apparent Power

## Apparent Power

Apparent power is the product of the rms value of voltage and the rms value of current. The **unit** of apparent power is called **VA (volt-ampere)**.

$$\boxed{S = VI} \quad (\text{volt-amperes, VA})$$

or, since

$$V = IZ \text{ and } I = \frac{V}{Z}$$

then

$$\boxed{S = I^2 Z} \quad (\text{VA})$$

and

$$\boxed{S = \frac{V^2}{Z}} \quad (\text{VA})$$

The average power to the load in Fig. 19.4 is

$$P = VI \cos \theta$$


However,

$$S = VI$$

Therefore,

$$\boxed{P = S \cos \theta} \quad (\text{W})$$

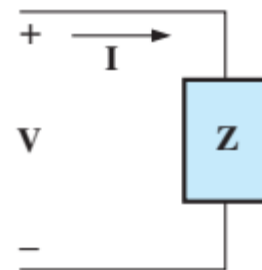and the power factor of a system  $F_p$  is



$$\boxed{F_p = \cos \theta = \frac{P}{S}} \quad (\text{unitless})$$

$$P = VI = S$$

$$F_p = \cos \theta = \frac{P}{S} = 1$$



# Inductive Circuit and Reactive Power

## Inductive Circuit and Reactive Power

For a purely inductive circuit  $v$  leads  $i$  by  $90^\circ$ , Substituting  $\theta = 90^\circ$

$$\begin{aligned} p_L &= VI \cos(90^\circ)(1 - \cos 2\omega t) + VI \sin(90^\circ)(\sin 2\omega t) \\ &= 0 + VI \sin 2\omega t \end{aligned}$$

$$p_L = VI \sin 2\omega t$$

where  $VI \sin 2\omega t$  is a sine wave with twice the frequency

*The net flow of power to the pure (ideal) inductor is zero over a full cycle, and no energy is lost in the transaction.*


We find that the instantaneous power can be written as:

$$p(t) = \underbrace{[V_{rms} I_{rms} \cos \theta](1 - \cos 2\omega t)}_{\text{Active Power}} + \underbrace{[V_{rms} I_{rms} \sin \theta] \sin 2\omega t}_{\text{Reactive Power}}$$

The peak or maximum value of instantaneous reactive power (or instantaneous reactive volt-ampere) is called the **reactive or imaginary or quadrature or wattless power** (or **reactive volt-ampere**).

The symbol for reactive power is  $Q$ , and its unit is the *volt-ampere reactive* (VAR).
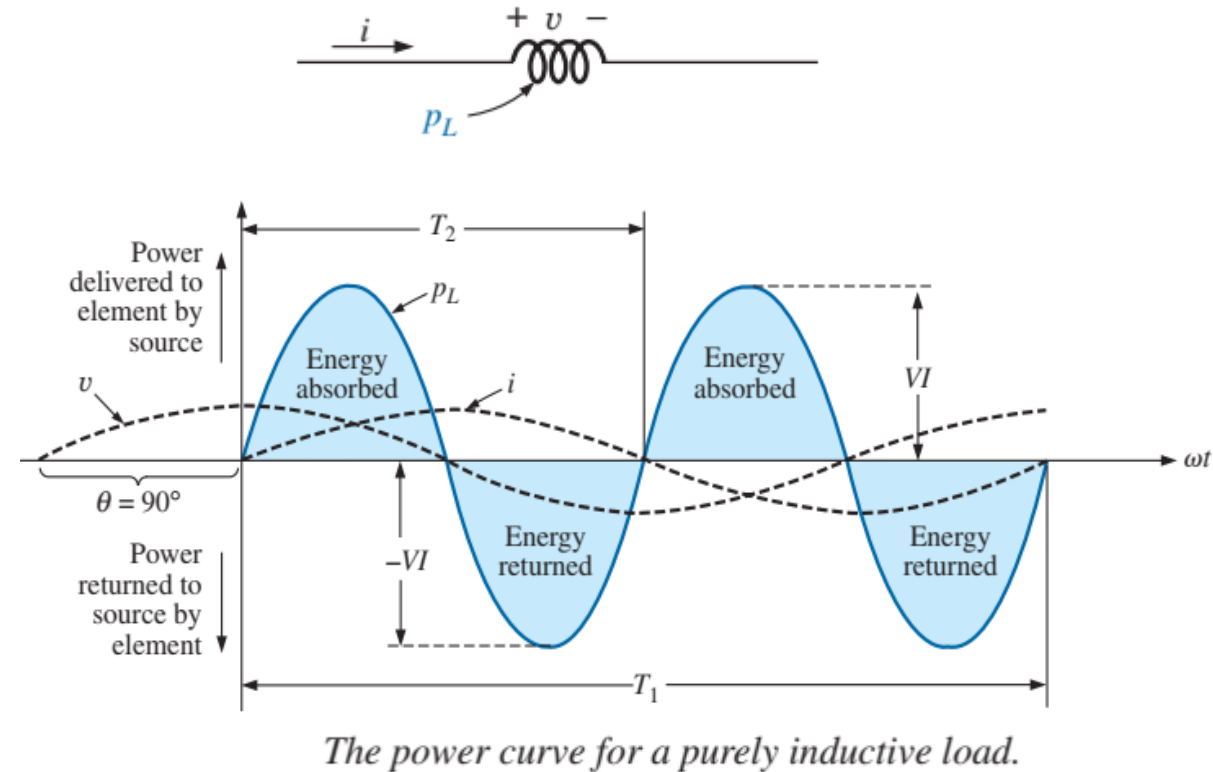
$$Q_L = VI \sin \theta \quad (\text{volt-ampere reactive, VAR}) \quad \text{where } \theta \text{ is the phase angle between } V \text{ and } I.$$





# Inductive Circuit and Reactive Power

## Inductive Circuit

$$Q_L = I^2 X_L$$

$$Q_L = \frac{V^2}{X_L}$$

The apparent power associated with an inductor is  $S = VI$ , and the average power is  $\overline{P} = 0$

$$F_p = \cos \theta = \frac{P}{S} = \frac{0}{VI} = 0$$

# Capacitive Circuit and Reactive Power

## Capacitive Circuit and Reactive Power

For a purely capacitive circuit  $i$  leads  $v$  by  $90^\circ$ ,

$$\theta = -90^\circ$$

$$\begin{aligned} p_C &= VI \cos(-90^\circ)(1 - \cos 2\omega t) + VI \sin(-90^\circ)(\sin 2\omega t) \\ &= 0 - VI \sin 2\omega t \end{aligned}$$

$$p_C = -VI \sin 2\omega t$$

where  $-VI \sin 2\omega t$  is a negative sine wave with twice the frequency

*The net flow of power to the pure (ideal) capacitor is zero over a full cycle,*

The reactive power associated with the capacitor is equal to the peak value of the  $p_C$  curve, as follows:



since  $V = IX_C$  and  $I = V/X_C$ ,

$$Q_C = I^2 X_C$$

$$Q_C = \frac{V^2}{X_C}$$

$$S = VI \quad (\text{VA})$$

and the average power is  $P = 0$ ,

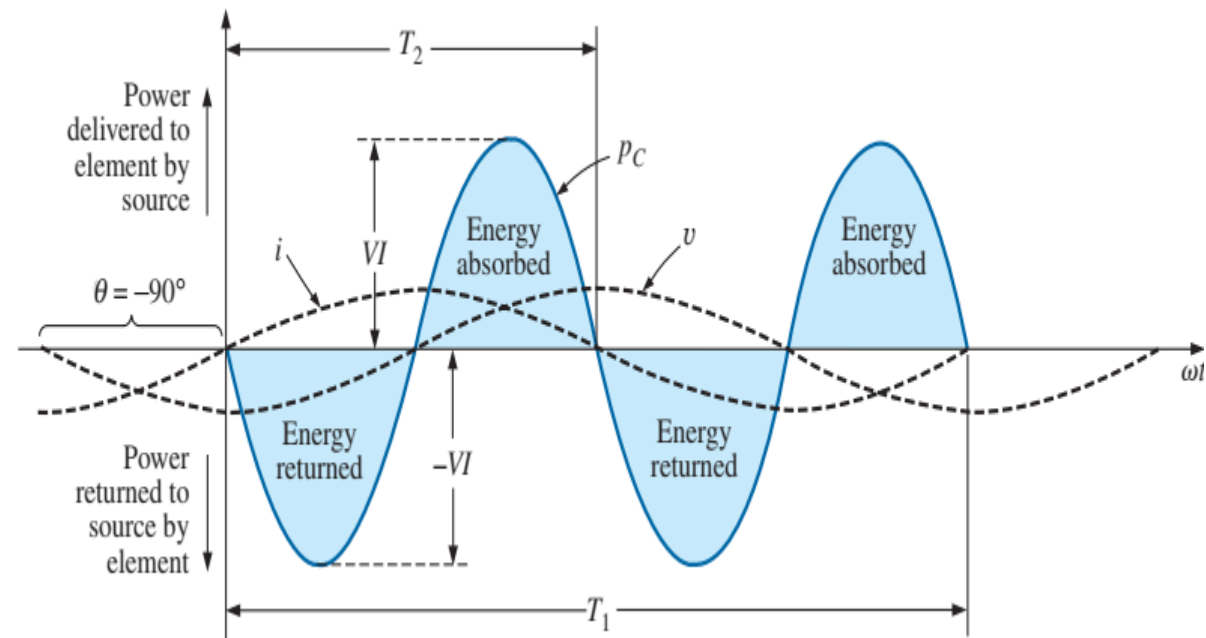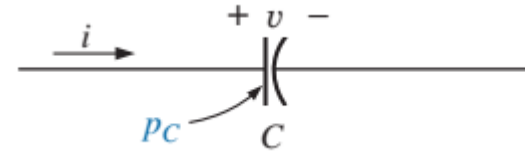

The apparent power associated with the capacitor is *The power curve for a purely capacitive load.*

# Capacitive Circuit and Reactive Power

For Capacitor

The apparent power associated with the capacitor is

$$S = VI \quad (\text{VA})$$

and the average power is  $P = 0$ ,

$$F_p = \cos \theta = \frac{P}{S} = \frac{0}{VI} = 0$$

# Instantaneous Equation of Power for R, L and C

Energy Stored:

**Resistor**


**Inductor or Choke**

**Capacitor or Condenser**

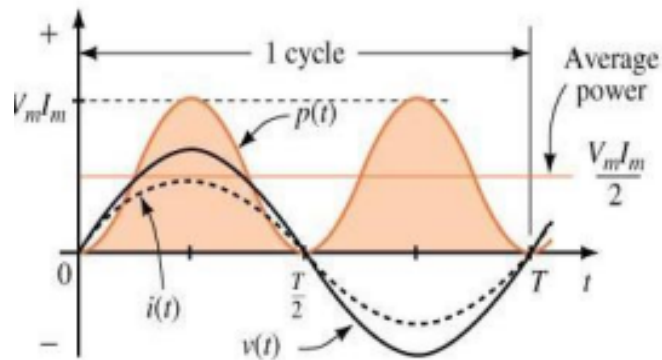**Instantaneous Power Equation:  $p(t) = P(1 - \cos 2\omega t) + Q \sin 2\omega t$**


$$p(t) = P(1 - \cos 2\omega t)$$

$$= V_{rms} I_{rms} (1 - \cos 2\omega t)$$




$$p(t) = Q \sin 2\omega t$$

$$= V_{rms} I_{rms} \sin 2\omega t$$

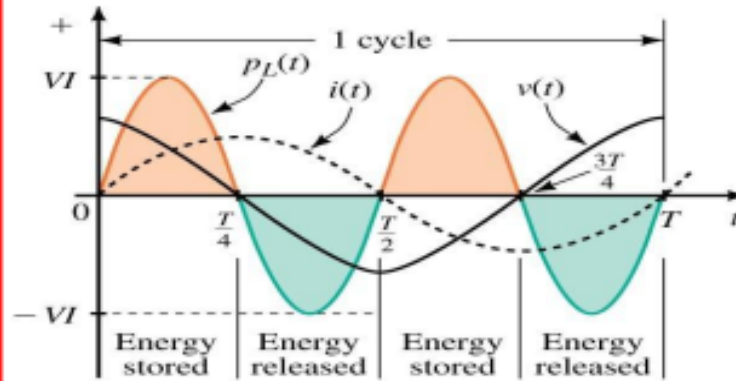

$$p(t) = Q \sin 2\omega t$$

$$= -V_{rms} I_{rms} \sin 2\omega t$$

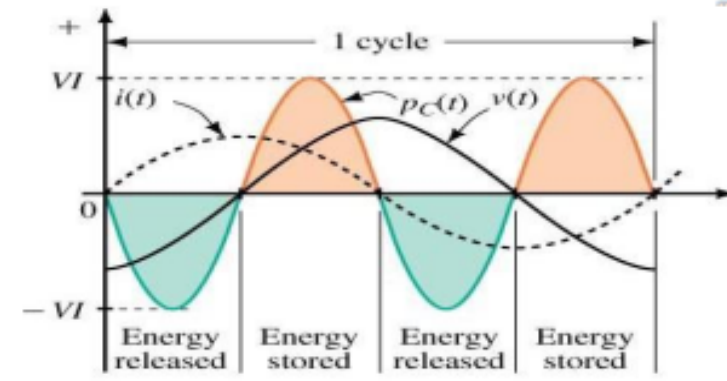

**Maximum Energy Stored by an Inductor:**

$$W_L = \int_0^{T/4} -\frac{V_m I_m}{2} \sin 2\omega t dt = \frac{V_m I_m}{4\omega} [\cos 2\omega t]_0^{T/4}$$

$$= \frac{V_m I_m}{2\omega} = \frac{\omega L I_m^2}{2\omega} = \frac{1}{2} L I_m^2 \text{ J}$$

**Maximum Energy Stored by a Capacitor:**

$$W_C = \int_0^{T/4} -\frac{V_m I_m}{2} \sin 2\omega t dt = \frac{V_m I_m}{4\omega} [\cos 2\omega t]_0^{T/4}$$

$$= \frac{V_m I_m}{2\omega} = \frac{\omega C V_m^2}{2\omega} = \frac{1}{2} C V_m^2 \text{ J}$$

# Power or Average Power

Real Power:

**Power (or Average or Real or Active or True or Wattfull Power)**

Since the average value of sine and cosine terms of instantaneous power are zero in one cycle, so the average power of instantaneous power can be written by:

$$P = P_{ave} = V_{rms} I_{rms} \cos \theta \quad [\text{W}]$$

$$P = I_{Rrms}^2 R = \frac{V_{Rrms}^2}{R} \quad [\text{W}]$$

The average power is also called *real or active or true or wattfull power or simply Power*.

The **unit** of real power is called **watt**. The real power is measured by **wattmeter**.

# Reactive Power or Reactive Volt-Amp

Reactive Power:

**Reactive or imaginary or Quadrature or Wattless Power (or Reactive Volt-Ampere)**

The peak or maximum value of instantaneous reactive power (or instantaneous reactive volt-ampere) is called the *reactive or imaginary or quadrature or wattless power* (or *reactive volt-ampere*).

The **unit** of reactive power is called **var** (reactive volt-ampere). The reactive power is measured by **varmeter**.

The reactive power or imaginary power or quadrature power or wattless power can be written as follows:

$$Q = P_x = V_{rms} I_{rms} \sin \theta = VI \sin \theta \text{ [var]}$$

$Q = 0$  for resistive load;  $Q > 0$  for inductive load;  $Q < 0$  for capacitive load

$$Q_L = I_{Lrms}^2 X_L = \frac{V_{Lrms}^2}{X_L} \text{ [var]}$$

$$Q_C = -I_{Crms}^2 X_C = -\frac{V_{Crms}^2}{X_C} \text{ [var]}$$

# Volt-Amp or Apparent Power

Volt-Amp.:

**Volt-Ampere or Apparent Power**

The apparent power can be obtained by combining the real and reactive power as follows:

$$S = \sqrt{P_r^2 + P_x^2} = \sqrt{P^2 + Q^2} = \frac{V_m I_m}{2} = V_{rms} I_{rms} = VI \text{ [VA]}$$

Apparent power is the product of the rms value of voltage and the rms value of current.

The **unit** of apparent power is called **VA (volt-ampere)**.

$$S = I_{rms}^2 Z_m = \frac{V_{rms}^2}{Z_m} \text{ [VA]}$$



# Power Factor and Power Factor Angle

Power Factor Leading or Lagging:

## Power Factor and Power Factor Angle

Cosine  $\theta$  ( $\cos\theta$ ) which is a factor, by which volt-amperes are multiplied to give power, is called power factor. Power factor is always **positive**. Power factor can be given by:

$$\text{Power Factor, } pf = \cos\theta = \frac{P}{V_{rms}I_{rms}} = \frac{P}{S}$$

**Power Factor Angle** is the phase difference between voltage and current.

$$\text{Power Factor Angle, } \theta = \theta_v - \theta_i$$

If voltage  $v(t)$  and current  $i(t)$  are **in phase**, power factor is **unity**.

Power factor **unity** means voltage  $v(t)$  and current  $i(t)$  are **in phase**.

If current  $i(t)$  **lags** voltage  $v(t)$ , power factor is **lagging**.

Power factor **lagging** means current  $i(t)$  **lags** voltage  $v(t)$ .

If current  $i(t)$  **leads** voltage  $v(t)$ , power factor is **leading**.

Power factor **leading** means current  $i(t)$  **leads** voltage  $v(t)$ .

# Reactive Factor

Reactive Factor:

## Reactive Factor

Sine  $\theta$  ( $\sin\theta$ ) which is a factor, by which volt-amperes are multiplied to give reactive power, is called reactive factor. Reactive factor may be **positive** or **negative**.

Reactive factor can be given by:

$$\text{Reactive Factor (rf)} = \sin\theta = \frac{Q}{V_{rms}I_{rms}} = \frac{Q}{S}$$

If voltage  $v(t)$  and current  $i(t)$  are **in phase**, reactive factor is **zero**.

Reactive factor **zero** means voltage  $v(t)$  and current  $i(t)$  are **in phase**.

If current  $i(t)$  **lags** voltage  $v(t)$ , reactive factor is **positive**.

Reactive factor **positive** means current  $i(t)$  **lags** voltage  $v(t)$ .

If current  $i(t)$  **leads** voltage  $v(t)$ , reactive factor is **negative**.

Reactive factor is **negative** means current  $i(t)$  **leads** voltage  $v(t)$ .

# Power Triangle

## Power Triangle:

### 19.7 THE POWER TRIANGLE

The three quantities **average power**, **apparent power**, and **reactive power** can be related in the vector domain by

$$\mathbf{S} = \mathbf{P} + \mathbf{Q} \quad (19.27)$$

with

$$\mathbf{P} = P \angle 0^\circ \quad \mathbf{Q}_L = Q_L \angle 90^\circ \quad \mathbf{Q}_C = Q_C \angle -90^\circ$$

For an inductive load, the *phasor power*  $\mathbf{S}$ , as it is often called, is defined by

$$\mathbf{S} = \mathbf{P} + j Q_L$$

as shown in Fig. 19.14.

The  $90^\circ$  shift in  $Q_L$  from  $P$  is the source of another term for reactive power: *quadrature power*.

For a capacitive load, the phasor power  $\mathbf{S}$  is defined by

$$\mathbf{S} = \mathbf{P} - j Q_C$$

as shown in Fig. 19.15.

If a network has both capacitive and inductive elements, the reactive component of the power triangle will be determined by the *difference* between the reactive power delivered to each. If  $Q_L > Q_C$ , the resultant

power triangle will be similar to Fig. 19.14. If  $Q_C > Q_L$ , the resultant power triangle will be similar to Fig. 19.15.

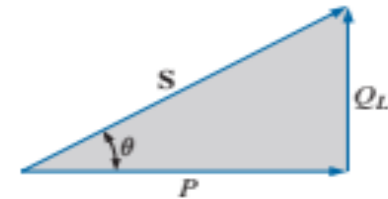


FIG. 19.14

Power diagram for inductive loads.

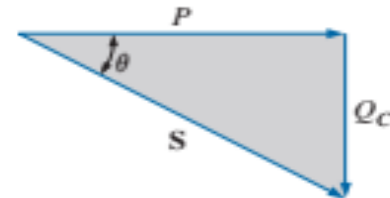


FIG. 19.15

Power diagram for capacitive loads.

# Example on Power Triangle

Example:

Consider, for example, the simple  $R$ - $L$  circuit in Fig. 19.19, where

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_T} = \frac{10 \text{ V} \angle 0^\circ}{3 \Omega + j 4 \Omega} = \frac{10 \text{ V} \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 2 \text{ A} \angle -53.13^\circ$$

The real power (the term *real* being derived from the positive real axis of the complex plane) is

$$P = I^2 R = (2 \text{ A})^2 (3 \Omega) = 12 \text{ W}$$

and the reactive power is

$$Q_L = I^2 X_L = (2 \text{ A})^2 (4 \Omega) = 16 \text{ VAR (L)}$$

with  $\mathbf{S} = P + j Q_L = 12 \text{ W} + j 16 \text{ VAR (L)} = 20 \text{ VA} \angle 53.13^\circ$

as shown in Fig. 19.20. Applying Eq. (19.29) yields

$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = (10 \text{ V} \angle 0^\circ)(2 \text{ A} \angle +53.13^\circ) = 20 \text{ VA} \angle 53.13^\circ$$

as obtained above.

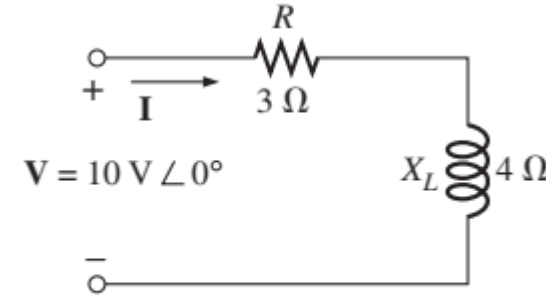


FIG. 19.19

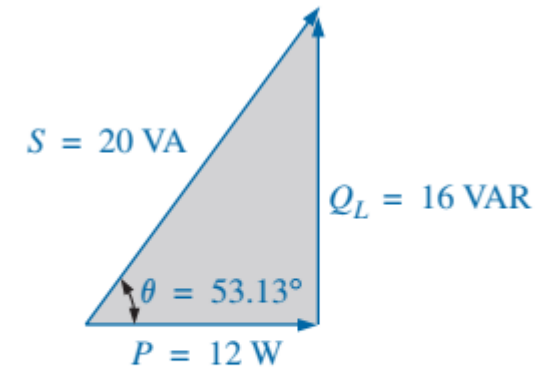


FIG. 19.20

The power triangle for the circuit in Fig. 19.19.

# Example on Power Calculation

Example:

**Example:** The voltage and current of a circuit are given as follows:  $v(t)=100\sin(314t+60^\circ)$  V and  $i(t)=10\sin(314t+30^\circ)$  A.

(i) Calculate the apparent power, the power or active power, the reactive power, the power factor, the reactive factor. (ii) Write the expression of instantaneous power. (iii) Draw the power triangle.

**Solution:** Here,  $\omega=314$  rad/s,  $V_m = 100$  V,  $I_m = 10$  A,  $\theta_v = 60^\circ$ , and  $\theta_i = 30^\circ$ .

Thus  $\theta = \theta_z = \theta_v - \theta_i = 60^\circ - 30^\circ = 30^\circ$ .

$$(i) S = V_{rms}I_{rms} = \frac{V_m I_m}{2} = \frac{100 \times 10}{2} = 500 \text{ VA} \quad \text{pf} = \cos \theta = \cos(30^\circ) = 0.866$$

$$\text{rf} = \sin \theta = \sin(30^\circ) = 0.5 \quad P = \frac{V_m I_m}{2} \cos \theta = \frac{100 \times 10}{2} \cos(30^\circ) = 433 \text{ W}$$


$$Q = \frac{V_m I_m}{2} \sin \theta = \frac{100 \times 10}{2} \sin(30^\circ) = 250 \text{ VAR}$$

# Example on Power Calculation

Power Calculation:

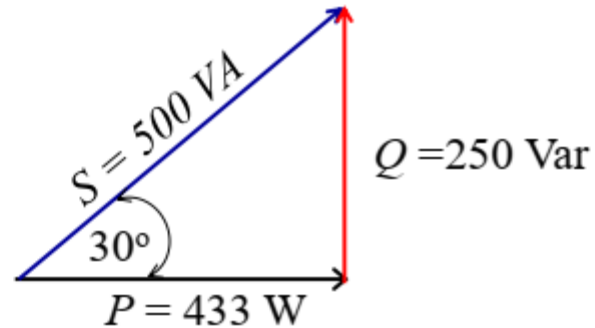(ii) The instantaneous real or active or true or wattfull power can be given by:

$$p(t) = P(1 - \cos 2\omega t) + Q \sin 2\omega t = 433(1 - \cos 628t) + 250 \cos 628t$$



**Power Triangle**

# Example of Power Calculation

Example:

**Example:** The voltage of  $v(t)=100\sin(314t-60^\circ)$  V applied to an impedance of  $Z=8.66 + j5$  ohm. (i) Calculate the apparent power, the power or active power, the reactive power, the power factor, the reactive factor. (ii) Write the expression of instantaneous power. (iii) Draw the power triangle.

**Solution:** Here,  $\omega=314$  rad/s,  $V_m = 100$  V,  $\theta_v = 60^\circ$

$$V = \frac{100}{\sqrt{2}} \angle 60^\circ = 70.7 \angle 60^\circ \text{ V}$$

$$Z = 8.66 + j5 = 10 \angle 30^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{70.7 \angle -60^\circ}{10 \angle 30^\circ} = 7.07 \angle -30^\circ \text{ A}$$

$$\theta = \theta_z = \theta_v - \theta_i = -60^\circ + 30^\circ = -30^\circ.$$

$$(i) S = V_{rms} I_{rms} = 70.7 \times 7.07 = 500 \text{ VA}$$

$$\text{pf} = \cos \theta = \cos(-30^\circ) = 0.866$$

$$\text{rf} = \sin \theta = \sin(-30^\circ) = -0.5$$

$$P = S \cos \theta = 500 \cos(-30^\circ) = 433 \text{ W}$$

$$Q = S \sin \theta = 500 \sin(-30^\circ) = -250 \text{ VAR}$$




# Example on Power Calculation

Power Triangle:

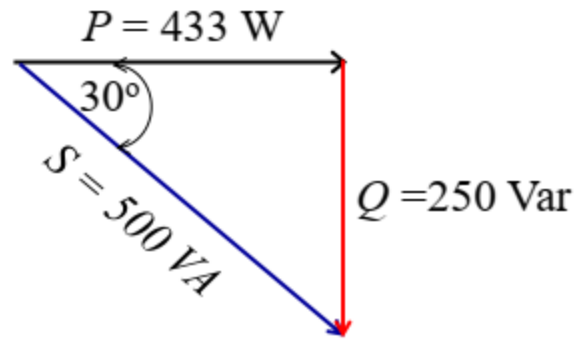(ii) The instantaneous real or active or true or wattfull power can be given by

$$p(t) = P(1 - \cos 2\omega t) + Q \sin 2\omega t = 433(1 - \cos 628t) + 250 \cos 628t$$



**Power Triangle**

# Complex Power


Complex Power:

## Complex Power

Let, voltage as a reference then the phasor diagram of voltage and current is as shown in the following figure.

Active Power :  $P = V(I \cos \theta)$

Reactive Power :  $Q = V(I \sin \theta)$

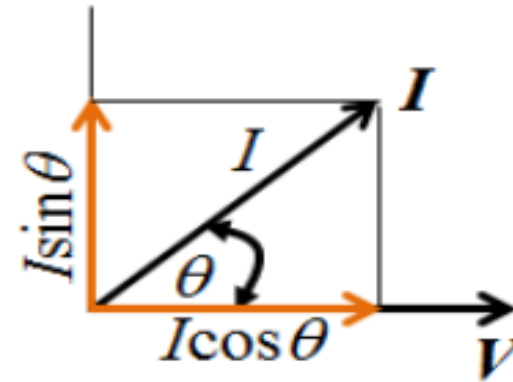

Since  $I \cos \theta$  is multiplied with  $V$  for active power, the component of current ( $I$ )  $I \cos \theta$  is called **active or real or true or wattfull component of current**.

Similarly, since  $I \sin \theta$  is multiplied with  $V$  for reactive power, the component of current ( $I$ )  $I \sin \theta$  is called **reactive or imaginary or quadrature or wattless component of current**.

# Voltage Current in Cartesian/Rectangular Form

Real/Reactive Power:

## Voltage and Current in Cartesian or Rectangular Form

**Voltage:**

$$V = V\angle\theta_v = V \cos \theta_v + jV \sin \theta_v = V_r + jV_i$$

$$V_r = V \cos \theta_v; \quad V_i = V \sin \theta_v$$

**Current:**

$$I = I\angle\theta_i = I \cos \theta_i + jI \sin \theta_i = I_r + jI_i$$

$$I_r = I \cos \theta_i; \quad I_i = I \sin \theta_i$$

## Real or Active Power

$$P = VI \cos \theta = VI \cos(\theta_v - \theta_i) = VI \cos \theta_v \cos \theta_i + VI \sin \theta_v \sin \theta_i$$

$$P = (V \cos \theta_v)(I \cos \theta_i) + (V \sin \theta_v)(I \sin \theta_i) = V_r I_r + V_i I_i$$

## Reactive Power

$$Q = VI \sin \theta = VI \sin(\theta_v - \theta_i) = VI \sin \theta_v \cos \theta_i - VI \cos \theta_v \sin \theta_i$$

$$Q = (V \sin \theta_v)(I \cos \theta_i) - (V \cos \theta_v)(I \sin \theta_i) = V_i I_r - V_r I_i$$

# Complex Power by Conjugate Method

Conjugate Method:


## Complex Power by Conjugate Current

According to the power triangle the complex power can be written as follows:

$$S = P + jQ = (V_r I_r + V_i I_i) + j(V_i I_r - V_r I_i)$$

$$S = P + jQ = (V_r + jV_i)(I_r - jI_i) = VI^*$$
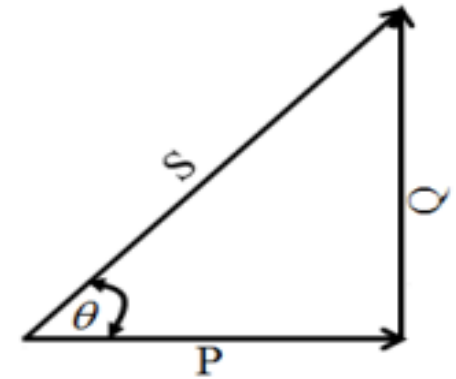
$$P = \text{Re}[S] = \text{Re}[VI^*]; \quad Q = \text{Im}[S] = \text{Im}[VI^*]$$



## Complex Power by Conjugate Voltage

$$S = P - jQ = (V_r I_r + V_i I_i) - j(V_i I_r - V_r I_i)$$

$$S = P - jQ = (V_r - jV_i)(I_r + jI_i) = V^* I$$

$$P = \text{Re}[S] = \text{Re}[V^* I]; \quad Q = -\text{Im}[S] = \text{Im}[V^* I]$$

# Complex Power by Conjugate Method

Example:

**Example:** The voltage and current of a circuit are given as follows:  $v(t)=100\sin(314t+60^\circ)$  V and  $i(t)=10\sin(314t+30^\circ)$  A.

Calculate the power or active power, the reactive power, the apparent power by using complex conjugate method by conjugation current.

**Solution:** Here,  $V_m = 100$  V,  $I_m = 10$  A,  $\theta_v = 60^\circ$ , and  $\theta_i = 30^\circ$ . Thus,

$$V = V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.7 \text{ V}$$

$$I = I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.07 \text{ A}$$

$$V = 70.7 \angle 60^\circ = 35.35 + j61.24 \text{ V}$$

$$I = 7.07 \angle 30^\circ = 6.122 + j3.535 \text{ A}$$

$$S = P + jQ = VI^* = (35.35 + j61.24)(6.122 - j3.535) = 433 + j250$$

$$P = \text{Re}[S] = \text{Re}[VI^*] = 433 \text{ W}; \quad Q = \text{Im}[S] = \text{Im}[VI^*] = 250 \text{ VAR}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{433^2 + 250^2} = 500 \text{ VA}$$

# Complex Power by Conjugate Method

Example:

**Example:** The voltage and current of a circuit are given as follows:  $V = 50\angle 30^\circ$  V and  $I = 5\angle 60^\circ$  A. Calculate the power or active power, the reactive power, the apparent power by using complex conjugate method by conjugation voltage.

**Solution:** Here,  $V_{rms} = 50$  V,  $I_{rms} = 5$  A,  $\theta_v = 30^\circ$ , and  $\theta_i = 60^\circ$ .

Thus  $\theta = \theta_z = \theta_v - \theta_i = 30^\circ - 60^\circ = -30^\circ$ .

$$V = 50\angle 30^\circ = 43.3 + j25 \text{ V}$$

$$I = 5\angle 60^\circ = 2.5 + j4.33 \text{ A}$$

$$S = P - jQ = V^* I = (43.3 - j25)(2.5 + j4.33) = 216.5 + j125$$

$$P = \text{Re}[S] = \text{Re}[V^* I] = 216.5 \text{ W}; \quad Q = -\text{Im}[S] = -\text{Im}[V^* I] = -125 \text{ VAR}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{216.5^2 + 125^2} = 250 \text{ VA}$$

# Power calculation RLC Series Circuit

Problem:

## EXAMPLE 19.4

- Find the total number of watts, volt-amperes reactive, and volt-amperes, and the power factor  $F_p$  for the network in Fig. 19.23.
- Sketch the power triangle.
- Find the energy dissipated by the resistor over one full cycle of the input voltage if the frequency of the input quantities is 60 Hz.
- Find the energy stored in, or returned by, the capacitor or inductor over one half-cycle of the power curve for each if the frequency of the input quantities is 60 Hz.

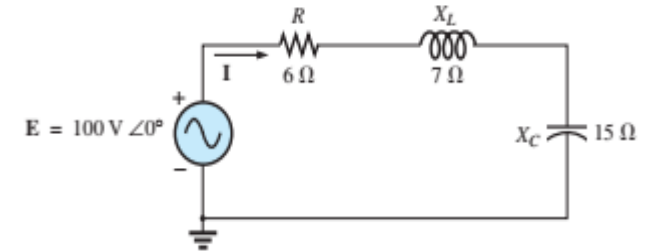


FIG. 19.23

Example 19.4.

## Solutions:

$$\begin{aligned}
 \text{a. } I &= \frac{E}{Z_T} = \frac{100 \text{ V } \angle 0^\circ}{6 \Omega + j7 \Omega - j15 \Omega} = \frac{100 \text{ V } \angle 0^\circ}{10 \Omega \angle -53.13^\circ} \\
 &= 10 \text{ A } \angle 53.13^\circ \\
 V_R &= (10 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) = 60 \text{ V } \angle 53.13^\circ \\
 V_L &= (10 \text{ A } \angle 53.13^\circ)(7 \Omega \angle 90^\circ) = 70 \text{ V } \angle 143.13^\circ \\
 V_C &= (10 \text{ A } \angle 53.13^\circ)(15 \Omega \angle -90^\circ) = 150 \text{ V } \angle -36.87^\circ \\
 P_T &= EI \cos \theta = (100 \text{ V})(10 \text{ A}) \cos 53.13^\circ = \mathbf{600 \text{ W}} \\
 &= I^2 R = (10 \text{ A})^2(6 \Omega) = \mathbf{600 \text{ W}} \\
 &= \frac{V_R^2}{R} = \frac{(60 \text{ V})^2}{6} = \mathbf{600 \text{ W}} \\
 S_T &= EI = (100 \text{ V})(10 \text{ A}) = \mathbf{1000 \text{ VA}} \\
 &= I^2 Z_T = (10 \text{ A})^2(10 \Omega) = \mathbf{1000 \text{ VA}} \\
 &= \frac{E^2}{Z_T} = \frac{(100 \text{ V})^2}{10 \Omega} = \mathbf{1000 \text{ VA}}
 \end{aligned}$$

$$\begin{aligned}
 Q_T &= EI \sin \theta = (100 \text{ V})(10 \text{ A}) \sin 53.13^\circ = \mathbf{800 \text{ VAR}} \\
 &= Q_C - Q_L \\
 &= I^2(X_C - X_L) = (10 \text{ A})^2(15 \Omega - 7 \Omega) = \mathbf{800 \text{ VAR}}
 \end{aligned}$$

$$\begin{aligned}
 Q_T &= \frac{V_C^2}{X_C} - \frac{V_L^2}{X_L} = \frac{(150 \text{ V})^2}{15 \Omega} - \frac{(70 \text{ V})^2}{7 \Omega} \\
 &= 1500 \text{ VAR} - 700 \text{ VAR} = \mathbf{800 \text{ VAR}}
 \end{aligned}$$

$$F_p = \frac{P_T}{S_T} = \frac{600 \text{ W}}{1000 \text{ VA}} = \mathbf{0.6 \text{ leading (C)}}$$

- b. The power triangle is as shown in Fig. 19.24.

$$\text{c. } W_R = \frac{V_R I}{f_1} = \frac{(60 \text{ V})(10 \text{ A})}{60 \text{ Hz}} = \mathbf{10 \text{ J}}$$

$$\text{d. } W_L = \frac{V_L I}{\omega_1} = \frac{(70 \text{ V})(10 \text{ A})}{(2\pi)(60 \text{ Hz})} = \frac{700 \text{ J}}{377} = \mathbf{1.86 \text{ J}}$$

$$W_C = \frac{V_C I}{\omega_1} = \frac{(150 \text{ V})(10 \text{ A})}{377 \text{ rad/s}} = \frac{1500 \text{ J}}{377} = \mathbf{3.98 \text{ J}}$$

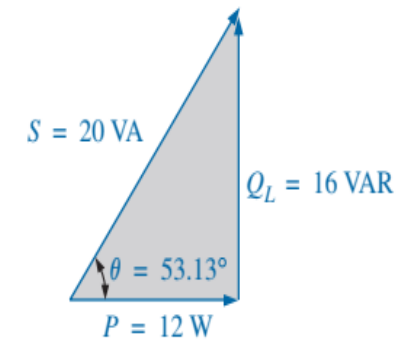


FIG. 19.20

The power triangle for the circuit in Fig. 19.19.



# Example Problem

Example:

**EXAMPLE 19.6** An electrical device is rated 5 kVA, 100 V at a 0.6 power-factor lag. What is the impedance of the device in rectangular coordinates?

**Solution:**

$$S = EI = 5000 \text{ VA}$$

Therefore, 
$$I = \frac{5000 \text{ VA}}{100 \text{ V}} = 50 \text{ A}$$

For  $F_p = 0.6$ , we have

$$\theta = \cos^{-1} 0.6 = 53.13^\circ$$


Since the power factor is lagging, the circuit is predominantly inductive, and  $\mathbf{I}$  lags  $\mathbf{E}$ . Or, for  $\mathbf{E} = 100 \text{ V} \angle 0^\circ$ ,

$$\mathbf{I} = 50 \text{ A} \angle -53.13^\circ$$

However,

$$\mathbf{Z}_T = \frac{\mathbf{E}}{\mathbf{I}} = \frac{100 \text{ V} \angle 0^\circ}{50 \text{ A} \angle -53.13^\circ} = 2 \Omega \angle 53.13^\circ = 1.2 \Omega + j 1.6 \Omega$$

which is the impedance of the circuit in Fig. 19.27.

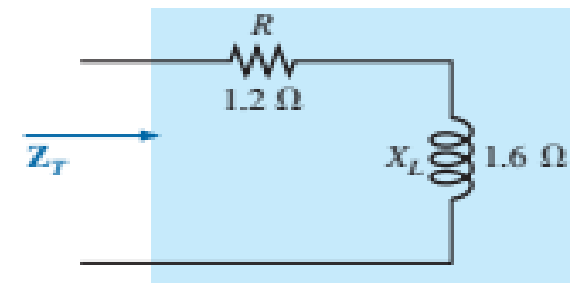

**FIG. 19.27**

*Example 19.6.*